



# MODULE 5 - DESIGN OF SEQUENTIAL LOGIC CIRCUITS

**Dr. E.Papanasam**


**[papanasam.e@vit.ac.in](mailto:papanasam.e@vit.ac.in)**

**AP Senior**

**School of Electronics**


**VIT Chennai**

# SEQUENTIAL CIRCUIT

 
 
# SR LATCH

- Asynchronous sequential circuits can be implemented by employing a basic flip-flop commonly referred to as an SR latch




$S$	$R$	$Q$	$Q'$	
1	0	1	0	
0	0	1	0	(After $SR = 10$ )
0	1	0	1	
0	0	0	1	(After $SR = 01$ )
1	1	0	0	

# FLIP-FLOP

- A flip-flop circuit can maintain a binary state indefinitely (as long as power is delivered to the circuit) until directed by an input signal to switch states
- The major differences among various types of flip-flops are in the number of inputs they possess and in the manner in which the inputs affect the binary state




# BASIC FLIP-FLOP CIRCUIT

 

(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$ )
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$ )
1	1	0	0

(b) Truth table

 


(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$ )
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$ )
0	0	1	1

(b) Truth table

# RS FLIP-FLOP

 


		SR			
		00	01	11	10
Q	0			X	1
	1	1		X	1

$\underbrace{\hspace{10em}}_R$


$$Q(t+1) = S + R'Q$$

Q	S	R	Q(t+1)
0	0	0	0
0	0	1	0
0		0	1
			Indeterminate
1			1
1	0	1	0
1	1	0	1
1	1	1	Indeterminate

 


 
# D FLIP-FLOP

- Eliminate the undesirable condition of the indeterminate state in the RS flip-flop
- Ensure inputs S and R are never equal to 1 at the same time



# D FLIP-FLOP

$Q$	$D$	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

  




# JK FLIP-FLOPS

- Refinement of the RS flip-flop
- Indeterminate state of the RS type is defined in the JK type
- Inputs J and K behave like inputs S and R to set and clear the flip-flop, respectively
- The input marked J is for set and the input marked K is for reset
- When both inputs J and K are equal to 1, the flip-flop switches to its complement state



# JK FLIP-FLOP

 

$Q$	$J$	$K$	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

(b) Characteristic table

		$J$			
		$JK$		11	10
$Q$	0			1	1
	1	1			1
		$K$			


$$Q(t+1) = JQ' + K'Q$$

# T FLIP-FLOPS

- Single-input version of the JK flip-flop
- T flip-flop is obtained from the JK flip-flop when both inputs are tied together
- The designation T comes from the ability of the flip-flop to "toggle," or complement, its state.
- Regardless of the present state, the flip-flop complements its output when the clock pulse occurs while input T is 1



# T FLIP-FLOPS

 

$Q$	$T$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

		0	$\overbrace{1}^T$
	0		1
$Q$	1	1	

$$Q(t+1) = TQ' + T'Q$$




# REGISTERS

- A register is a group of binary cells suitable for holding binary information.
- A group of flip-flops constitutes a register, since each flip-flop is a binary cell capable of storing one bit of information
- An n-bit register has a group of n flip-flops and is capable of storing any binary information containing n bits
- In addition to the flip-flops, a register may have combinational gates that perform certain data-processing tasks
- Register consists of a group of flip-flops and gates that affect their transition
- The flip-flops hold binary information and the gates control when and how new information is transferred into the register.



# 4-BIT REGISTER

 

# SHIFT REGISTERS

## Register:

- A set of  $n$  flip-flops

- Each flip-flop stores one bit


- Two basic functions: data storage and data movement

## Shift Register:


- A register that allows each of the flip-flops to pass the stored information to its adjacent neighbour




# BASIC DATA MOVEMENT IN SHIFT REGISTERS

 


(a) Serial in/shift right/serial out

 


(b) Serial in/shift left/serial out

 


(c) Parallel in/serial out

 


(d) Serial in/parallel out

 

(e) Parallel in/parallel out

 

(f) Rotate right

 


(g) Rotate left




 
# SHIFT REGISTERS

- A register capable of shifting its binary information either to the right or to the left is called a shift register
- The logical configuration of a shift register consists of a chain of flip-flops connected in cascade, with the output of one flip-flop connected to the input of the next flip-flop
- All flip-flops receive a common clock pulse that causes the shift from one stage to the next




# SHIFT REGISTERS (SISO)


- The Q output of a given flip-flop is connected to the D input of the flip-flop at its right
- Each clock pulse shifts the contents of the register one bit position to the right
- The **serial input** determines what goes into the leftmost flip-flop during the shift
- The **serial output** is taken from the output of the rightmost flip-flop
- Applications: Ring counter



 
# TIMING DIAGRAM OF 4-BIT SISO SHIFT REGISTER




# SERIAL IN PARALLEL OUT (SIPO)

 


# SERIAL IN PARALLEL OUT (SIPO)

 


# 4-BIT PISO SHIFT REGISTER

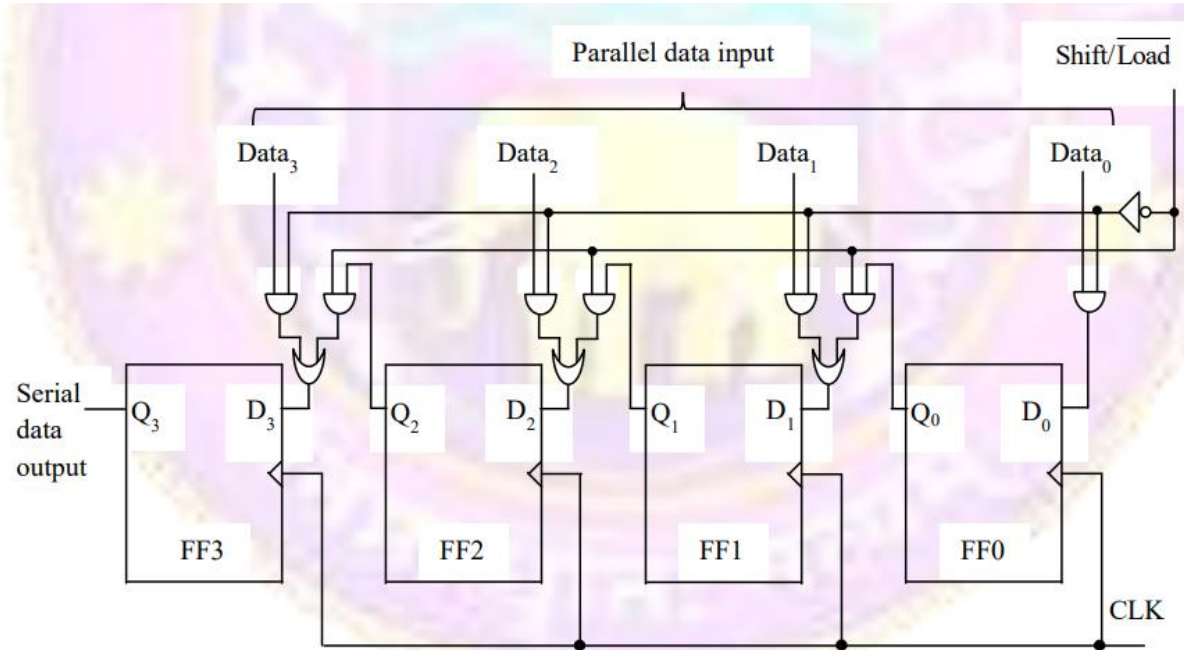

# PISO

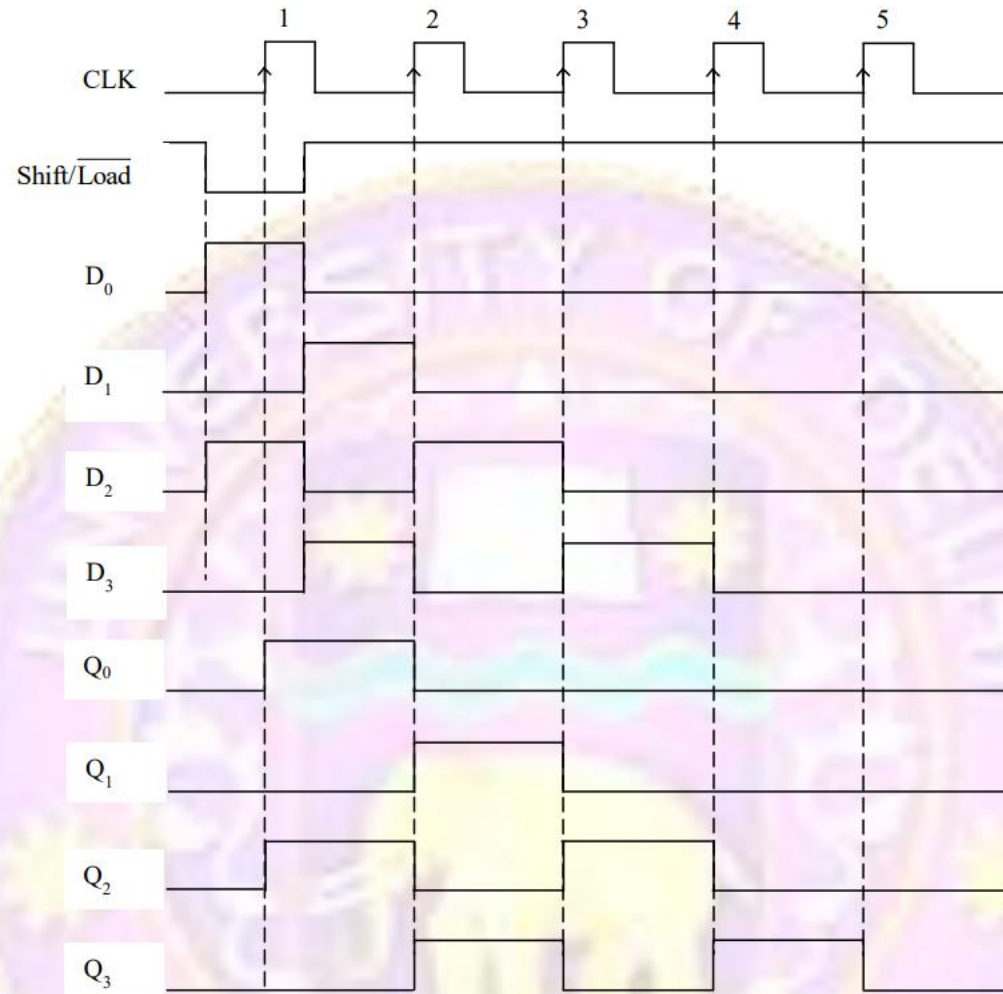


# PARALLEL IN PARALLEL OUT (PIPO)

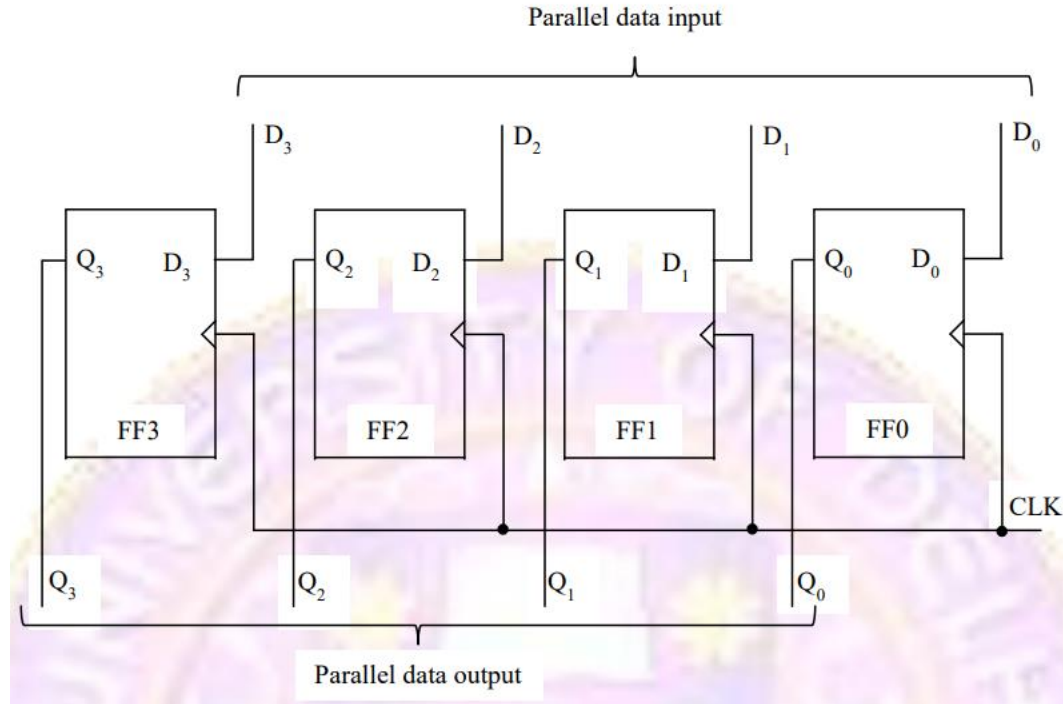



# PIPO

 

# COUNTERS

- A sequential circuit that goes through a prescribed sequence of states upon the application of input pulses
- The input pulses, called count pulses, may be clock pulses or they may originate from an external source and may occur at prescribed intervals of time or at random
- In a counter, the sequence of states may follow a binary count or any other sequence of states
- Counters are found in almost all equipment containing digital logic.
- Used for counting the number of occurrences of an event
- Useful for generating timing sequences to control operations in a digital system

# BINARY COUNTER

- A counter that follows the binary sequence is called a binary counter
- An n-bit binary counter consists of n flip-flops and can count in binary from 0 to  $2^{n-1}$



# DESIGN OF SYNCHRONOUS SEQUENTIAL CIRCUIT

- The design of a clocked sequential circuit starts from
  - a set of specifications and culminates in a logic diagram
  - or
  - a list of Boolean functions from which the logic diagram can be obtained
- Sequential circuit requires a state table for its specification
- The first step in the design of sequential circuits is to obtain a state table or an equivalent representation state diagram




# DESIGN OF SYNCHRONOUS SEQUENTIAL CIRCUIT

- A synchronous sequential circuit is made up of flip-flops and combinational gates
- The design of the circuit consists of choosing the flip-flops and then finding a combinational gate structure that, together with the flip-flops, produces a circuit that fulfills the stated specifications
- The number of flip-flops is determined from the number of states needed in the circuit



# DESIGN OF 3-BIT BINARY UP COUNTER

## State diagram and Excitation Table



 


Present State			Next State			Flip-Flop Inputs		
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$TA_2$	$TA_1$	$TA_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

State  
Table



# DESIGN OF 3-BIT BINARY COUNTER

## ○ K-map

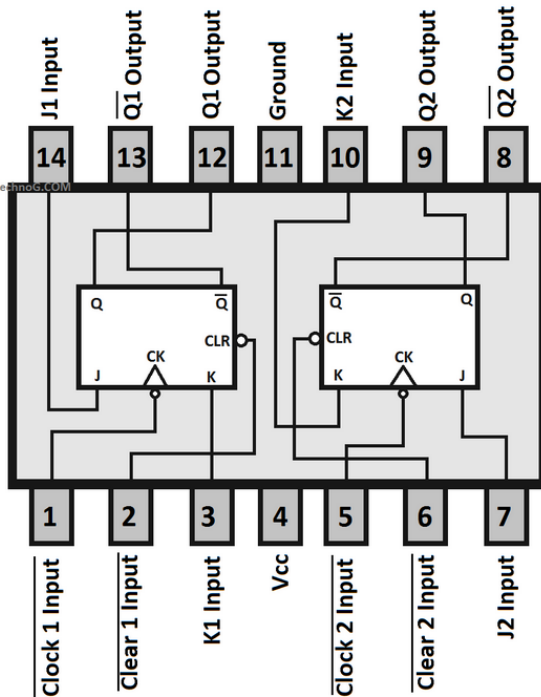  


IC 7473 Pinout Diagram

## 2-bit ASynch Binary counter

  




### 3-Bit Asynch Binary Counter

 


# Binary state seq.

Clock pulse	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
Initial state	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

# DECADE CONTER

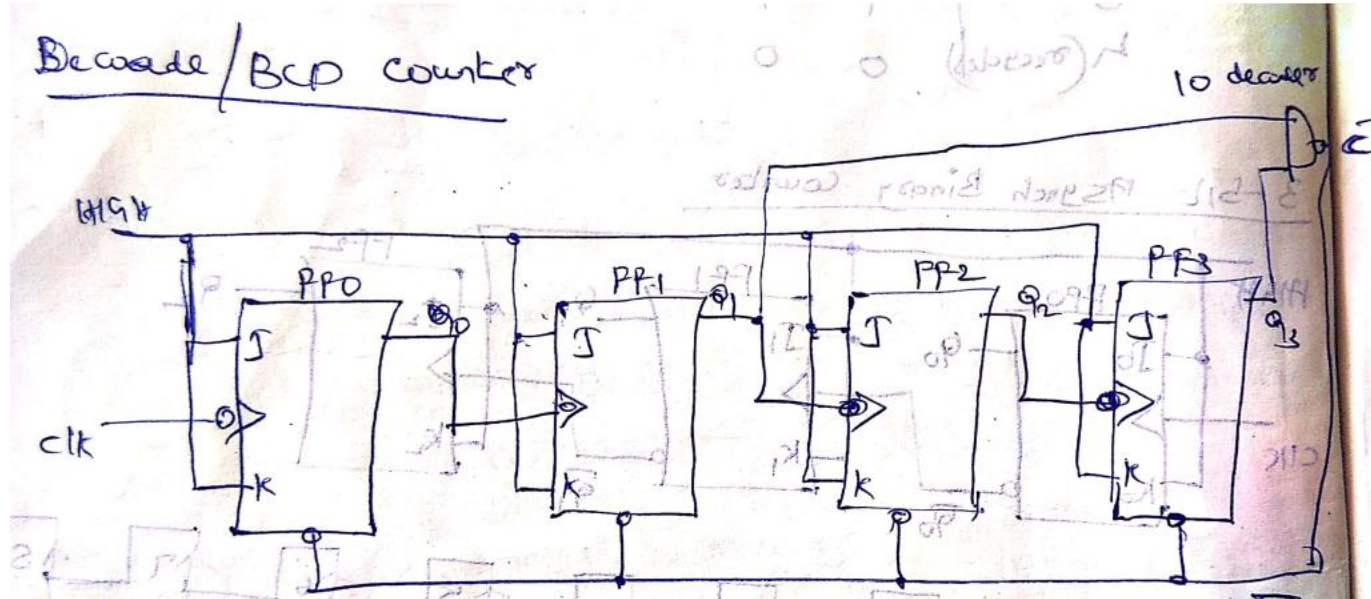

 




# RING COUNTER


- Developed by modifying a shift register
- Used in digital system to generate control pulses.
- A typical 4-bit ring counter is made of D-flip flops or JK-flip flop connected in cascade with the non-complemented output of the last stage connected as an input to the first stage.
- There are **no external inputs except the clock signal**
- Ring counter has **Mod = n** '**n**' is the number of bits
- It means 4-bit ring counter has 4 states
- Divides the frequency of the clock signal by 'n'.
- n is the bit size of the ring counter.
- Can be used as a frequency divider



# RING COUNTER

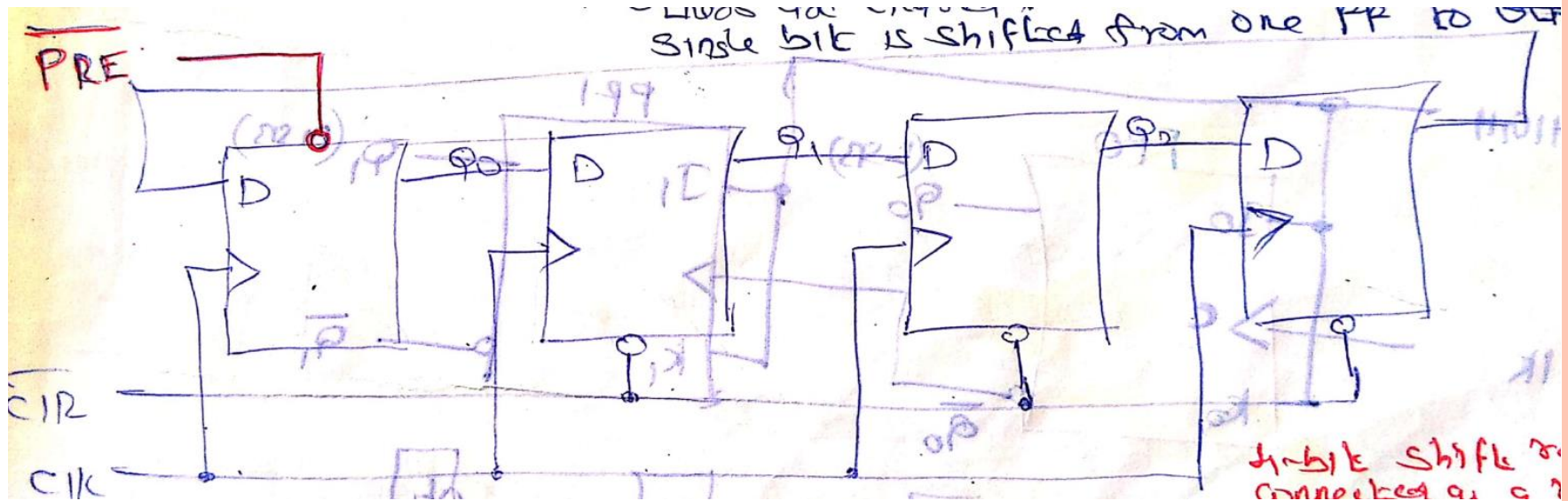


States	$Q_A$	$Q_B$	$Q_C$	$Q_D$
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1

 
 
# JOHNSON COUNTER

- Default state of Johnson counter is 0000






States	$Q_A$	$Q_B$	$Q_C$	$Q_D$
1	0	0	0	0
2	1	0	0	0
3	1	1	0	0
4	1	1	1	0
5	1	1	1	1
6	0	1	1	1
7	0	0	1	1
8	0	0	0	1


 
# JOHNSON COUNTER

- More outputs as compared to ring counter.
- It has same number of flip flop but it can count twice the number of states the ring counter can count.
- It count the data in a continuous loop
- It only needs half the number of flip-flops compared to the standard ring counter for the same MOD
- Divides a clock signal's frequency by '2n'.
- n is the bit size of the counter.
- Johnson counter uses less number of flip-flops compare to a typical ring counter.





# VERILOG MODELING - DESIGN BLOCK

- **module** up\_counter(**input** clk, reset,  
    **output**[3:0] counter );
- **reg** [3:0] counter\_up; // up counter
- **always** @(posedge clk or posedge reset)
- **begin** if(reset) counter\_up <= 4'd0;
- **else** counter\_up <= counter\_up + 4'd1;
- **end**
- **assign** counter = counter\_up;
- **endmodule**



# TEST BENCH

- **module** upcounter\_testbench();
- **reg** clk, reset;
- **wire** [3:0] counter;
- up\_counter dut(clk, reset, counter);
- **Initial**
- **begin**
  - clk=0;
  - **forever** #5 clk=~clk;
- **end**
- **initial**
- **begin**
  - reset=1;
  - #20; reset=0;
- **end**
- **endmodule**



- **module** down\_counter(**input** clk, reset, **output** [3:0] counter );
- **reg** [3:0] counter\_down; // down counter
- **always** @(posedge clk or posedge reset)
- **begin**
- **if**(reset) counter\_down <= 4'hf;
- **else** counter\_down <= counter\_down - 4'd1;
- **end**
- **assign** counter = counter\_down;
- **endmodule**



- **module** downcounter\_testbench();
- **reg** clk, reset;
- **wire** [3:0] counter;
- down\_counter dut(clk, reset, counter);
- **initial**
- **begin**
- clk=0;
- **forever** #5 clk=~clk;
- **end**
- **initial**
- **begin**
- reset=1; #20; reset=0;
- **end**
- **endmodule**



- **module** up\_down\_counter(**input** clk, reset, up\_down, **output**[3:0] counter );
- **reg** [3:0] counter\_up\_down; // down counter **always** **@(posedge** clk **or posedge** reset)
- **begin** **if**(reset) counter\_up\_down <= 4'h0;
- **else if**(~up\_down)
- counter\_up\_down <= counter\_up\_down + 4'd1;
- **else** counter\_up\_down <= counter\_up\_down - 4'd1;
- **end**
- **assign** counter = counter\_up\_down;
- **endmodule**





- **module** updowncounter\_testbench;
- **reg** clk, reset, up\_down;
- **wire** [3:0] counter;
- up\_down\_counter dut(clk, reset, up\_down, counter);
- **initial**
- **begin**
  - clk=0; forever #5 clk=~clk;
- **end**
- **initial**
- **begin**
  - reset=1; up\_down=0;
  - #20; reset=0; #200; up\_down=1;
- **end**
- **endmodule**



## 4 BIT JOHNSON COUNTER:

- **module** johnson\_counter(Clock, Reset, Count\_out);  
  **input** Clock,Reset;  
  **output** [3:0] Count\_out;  
  **reg** [3:0] Count\_temp;
- **always** @(posedge(Clock) or Reset)  
  **begin**  
    **if**(Reset == 1'b1)
- **begin**
- Count\_temp = 4'b0000;
- **end**
- **else if**(Clock == 1'b1)
- **begin**
- Count\_temp = {~Count\_temp[0],Count\_temp[3:1]}; **end**
- **end**  
    //The Count value is assigned to final output port.  
    **assign** Count\_out = Count\_temp;
- **endmodule**



# RIPPLE COUNTER

```
module dff (    input d,
               input clk,
               input rstn,
               output reg q,
               output qn);
    always @ (posedge clk or negedge rstn)
        if (!rstn)
            q <= 0;
        else
            q <= d;

    assign qn = ~q;
endmodule
```

```
module ripple ( input clk,
                input rstn,
                output [3:0] out);

    wire q0;
    wire qn0;
    wire q1;
    wire qn1;
    wire q2;
    wire qn2;
    wire q3;
    wire qn3;
```

```
    dff    dff0 ( .d (qn0),
                  .clk (clk),
                  .rstn (rstn),
                  .q (q0),
                  .qn (qn0));

    dff    dff1 ( .d (qn1),
                  .clk (q0),
                  .rstn (rstn),
                  .q (q1),
                  .qn (qn1));
```

```
    dff    dff2 ( .d (qn2),
                  .clk (q1),
                  .rstn (rstn),
                  .q (q2),
                  .qn (qn2));
```

```
    dff    dff3 ( .d (qn3),
                  .clk (q2),
                  .rstn (rstn),
                  .q (q3),
                  .qn (qn3));
```

```
    assign out = {qn3, qn2, qn1, qn0};

endmodule
```



- <https://www.fpga4student.com/2017/03/verilog-code-for-counter-with-testbench.html>
- <https://verilogcodes.blogspot.com/2015/10/verilog-code-for-4-bit-johnson-counter.html>
- <https://www.chipverify.com/verilog/verilog-ripple-counter-dff>

